



LAND OF THE CURIOUS



ENGINEERING PHYSICS 30.9.2021

LECTURE 4: CIRCUITS AND DC INSTRUMENTS

Subtitle


Name

Aleksi Mankonen

Title | Organisation

Associate professor

DC CIRCUIT

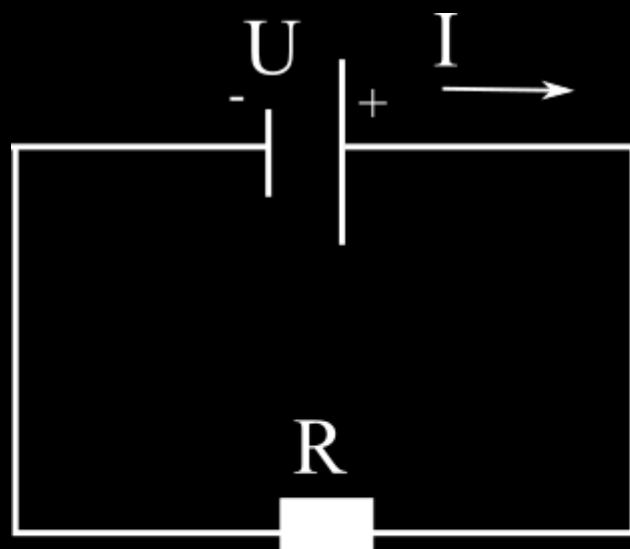


U Voltage
 $[U] = \text{V}$ Volt

R Resistance
 $[R] = \Omega$ Ohm

I Electrical current
 $[I] = \text{Ampere}$

ALTERNATIVE NOTATION FOR RESISTANCE

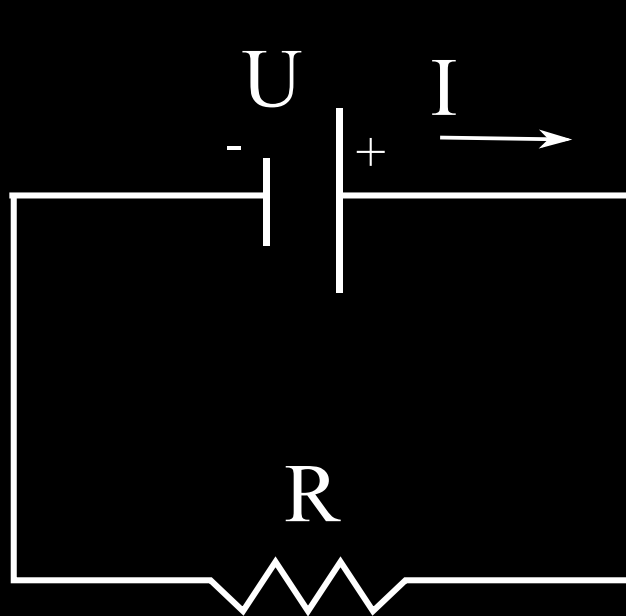

U Voltage

$[U] = V$ Volt


R Resistance

$[R] = \Omega$ Ohm

I Electrical current


$[I] =$ Ampere

OHM'S LAW

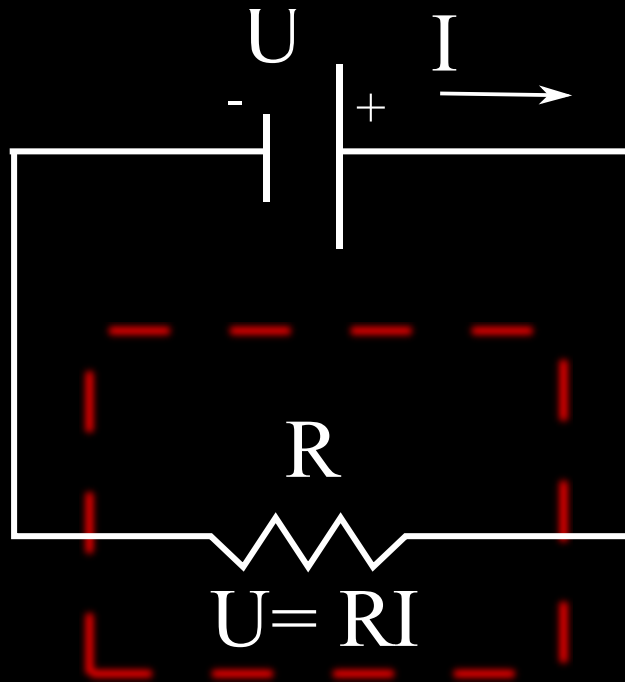

$$U = RI$$

OHM'S LAW- RESISTANCES IN SERIES

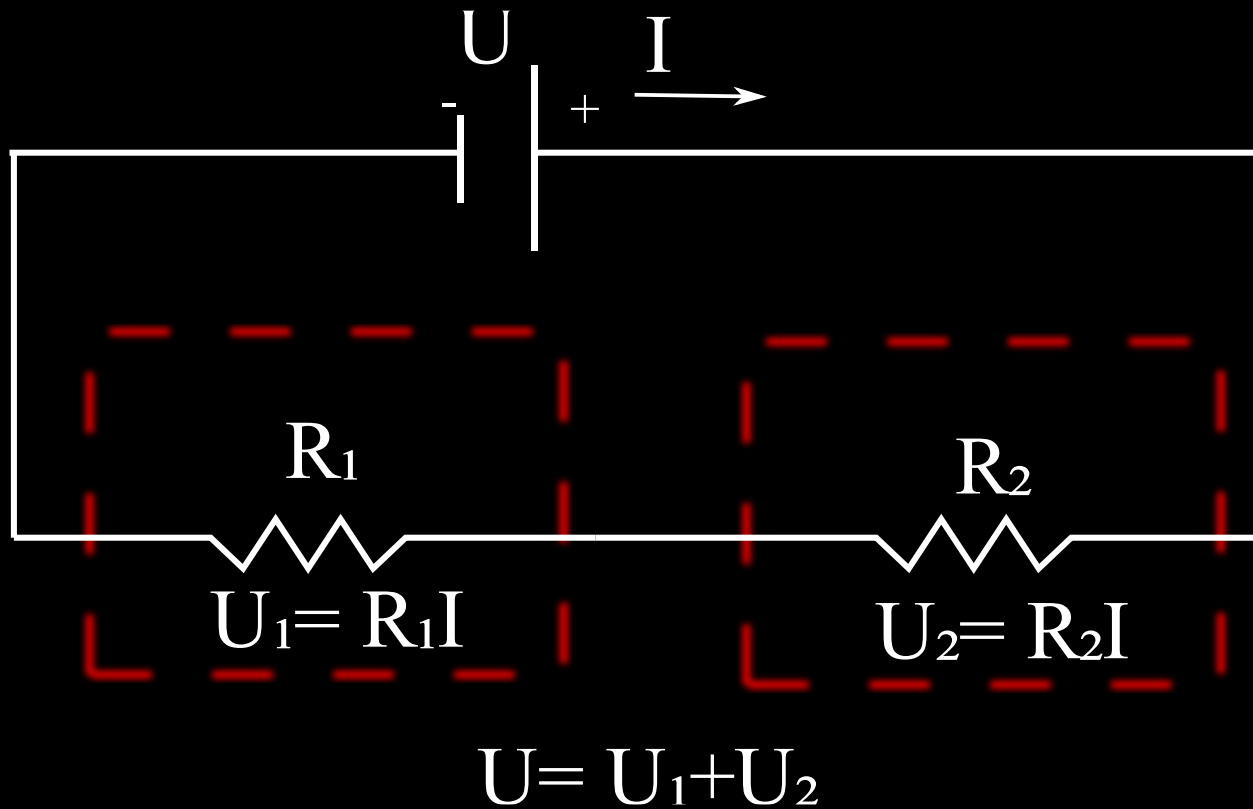


OHM'S LAW- PARALLEL RESISTANCES

$$I = I_1 + I_2 = \frac{U}{R_1} + \frac{U}{R_2} = \frac{U}{R}$$


$$\frac{R}{U} = \frac{1}{U \left(\frac{1}{R_1} + \frac{1}{R_2} \right)}$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$
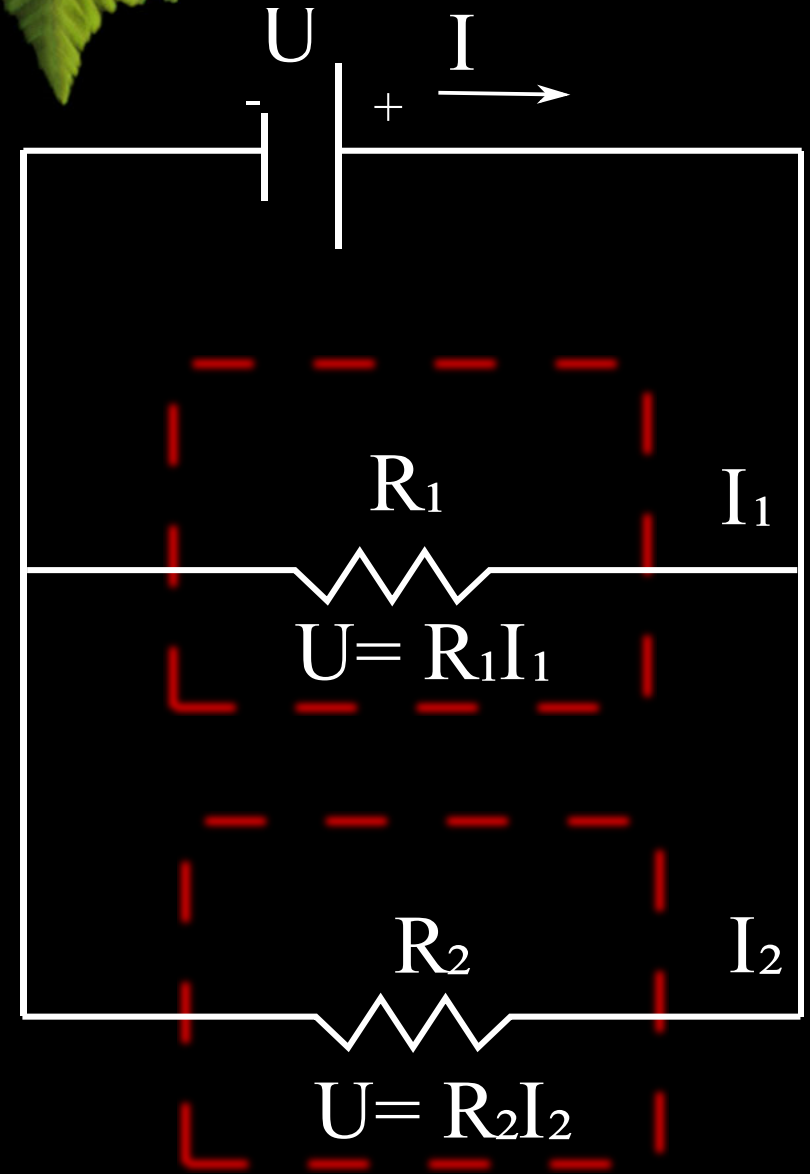
$$R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$



JOULE'S LAW

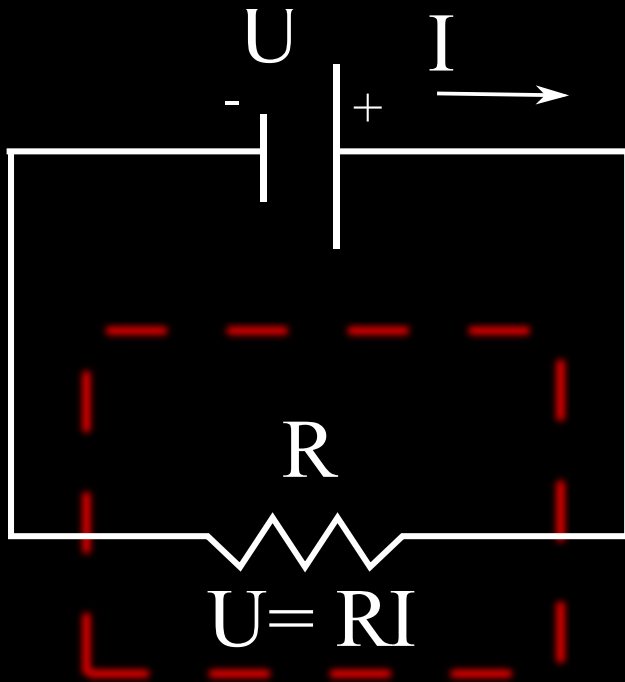

$$U = RI$$

$$P = UI$$

$$[P] = W$$

$$U = RI$$

$$P = RI^2$$


$$P = \frac{U^2}{R}$$

JOULE'S LAW

$$P_1 = R_1 I^2$$

$$P_2 = R_2 I^2$$

$$P = (R_1 + R_2) I^2$$

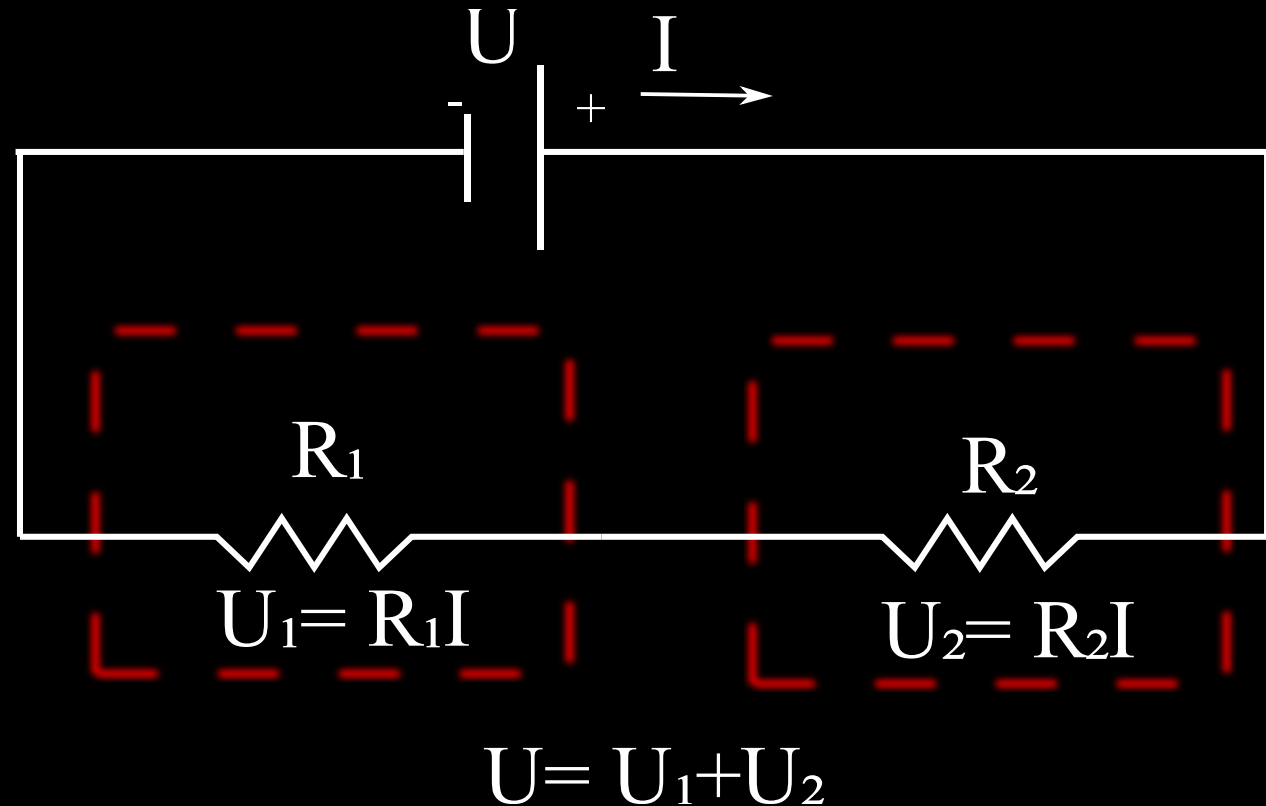



ELECTROMOTIVE FORCE - EMF

- » Ideal voltage that the device creates without any resistances
- » Device itself has an internal resistance
- » 1.5 V battery has terminal voltage of 1.5 V, but the electromotive force is more than that
- » Denoted by \mathcal{E}
- » $[\mathcal{E}] = \text{V}$ Volt

INTERNAL RESISTANCE

- » Internal resistance
- » U – Terminal voltage

