

Logic circuits and functions

Olli-Pekka Hämmäläinen

Control logic



- ▶ In modern machines, the vast majority of control & information transfer processes are done in digital fashion
- ▶ The control is practically implemented via logic gates
- ▶ These gates are basically propositions connected by connectives
 - ▶ We are already familiar with most of these
- ▶ Gates are constructed from simple electrical parts: diodes, transistors and relays
- ▶ Control is based on Boolean algebra

Boolean algebra

- ▶ In Boolean algebra, variables have only a truth value (1/0, or TRUE / FALSE, respectively)
- ▶ The basic Boolean functions are the same as the connectives in propositional logic:
 - ▶ Conjunction ($a \wedge b$)
 - ▶ Disjunction ($a \vee b$)
 - ▶ Negation ($\neg a$)
- ▶ In Boolean algebra, following simplified shorthand notation is often used:
 - ▶ Conjunction ab (AND = Boolean multiplication)
 - ▶ Disjunction $a + b$ (OR = Boolean addition)
 - ▶ Negation \bar{a} or alternatively a'

Boolean algebra

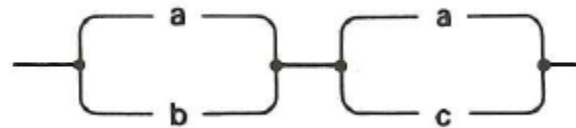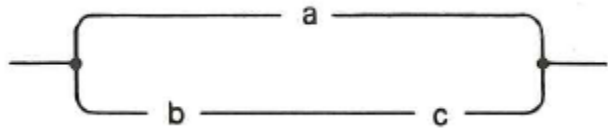- ▶ In Boolean algebra, it is important to notice the following peculiarities:
 - ▶ $1 + 1 = 1$ (OR)
 - ▶ $a + bc = (a + b)(a + c)$
- ▶ Both of these seem to be against the rules of “regular” algebra, but these rules can be shown to be correct by
 - ▶ Constructing a truth table
 - ▶ Sketching the graphs of these circuits




Logic gates

- ▶ Logic gates have their own drawing symbols


- ▶ Left: American version (more common)

- ▶ Right: European version


- ▶ AND

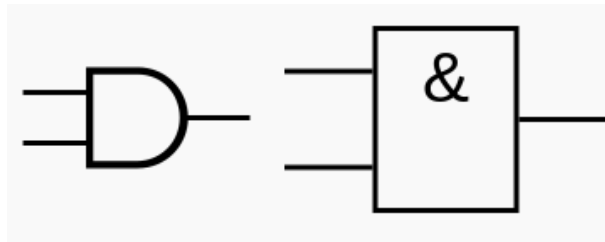

- ▶ OR

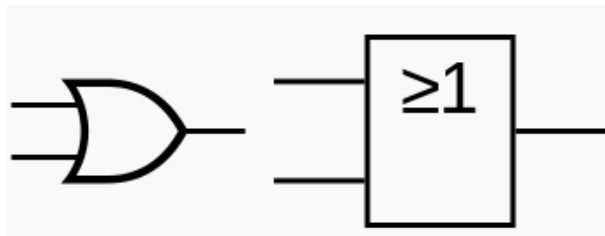

- ▶ NOT

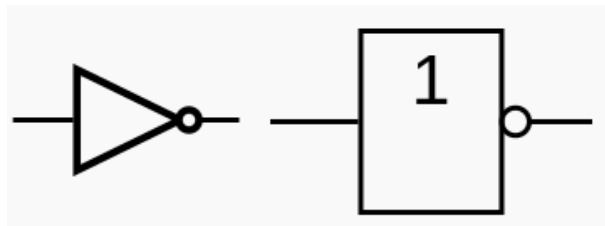

Simplified circuit diagram

- ▶ A logic circuit can be drawn also without “fancy” symbols using just a simple basic idea:
 - ▶ Draw all possible situations where the truth value is 1 - so, a signal can travel from left to right
 - ▶ Current values of variables are indicated by variable letters and their negations as in shorthand notation

- ▶ AND = series



$$F = ab$$

- ▶ OR = parallel



$$F = a + b$$


- ▶ NOTE: This notation only allows negations of sole variables, so we might have to use De Morgan's laws

$$\overline{ab} \Leftrightarrow \bar{a} + \bar{b}$$

$$\overline{a + b} \Leftrightarrow \bar{a}\bar{b}$$

Simplified circuit diagram

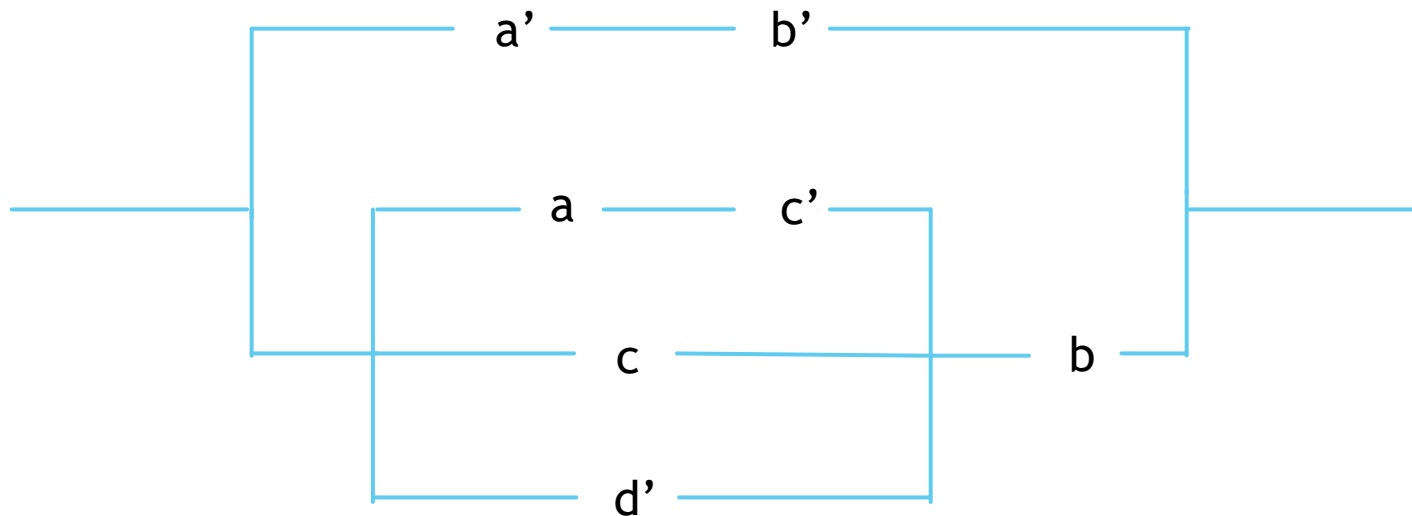- ▶ Simplified circuit diagram is often easier to understand for people who are not familiar with electronics, computer science or advanced mathematics
- ▶ Example:



- ▶ Logic function: $a'b' + (ac' + c + d')b$
- ▶ Expanded SOP-form: $a'b' + abc' + bc + bd'$

Forms of logic function

- ▶ The switching logic can be presented in three forms:
 - ▶ Truth table (we've done these already)
 - ▶ Logic function in Boolean algebra
 - ▶ Circuit diagram (official or simplified)
- ▶ The logic function can be constructed in two different normal forms:
 - ▶ Disjunctive normal form DNF (Sum Of Products, SOP)
 - ▶ Conjunctive normal form CNF (Product Of Sums, POS)
- ▶ The difference is significant

Sum of Products (SOP)

- ▶ In SOP-form the logic function is constructed of products of which each of them gives a truth value of 1
- ▶ A product term which includes all the variables is called a minterm
- ▶ One minterm corresponds to exactly one combination in the truth table; for this combination the minterm gets a truth value of 1 and all other combinations cause the minterm go to 0
- ▶ Summing up all the minterms produces a standard SOP form for the circuit
- ▶ In computer science this form is called disjunctive normal form (DNF)
- ▶ A SOP-circuit always has two levels:
 - ▶ First all AND operations
 - ▶ In the end all OR operations (between minterms)

Product of Sums (POS)

- ▶ In POS-form the logic function is constructed of sum terms of which each of them gives a truth value of 0
- ▶ A sum term which includes all the variables is called a maxterm
- ▶ NOTE! Now the negations in maxterms are inverted, because the truth value must be zero!
 - ▶ For example, if in truth table the truth value of A is 1, we have to write the negation of A in the sum term; see example on next slide)
- ▶ Multiplying all the maxterms produces a standard POS form for the circuit
- ▶ In computer science this form is called conjunctive normal form (CNF)
- ▶ A POS-circuit always has two levels, too:
 - ▶ First all OR operations
 - ▶ In the end all AND operations (between maxterms)

Minterms and maxterms

- ▶ Example of minterms and maxterms in a three-variable circuit case:

X Y Z	Minterms		Maxterms	
	Product	Symbol	Sum	Symbol
0 0 0	$\bar{X}\bar{Y}\bar{Z}$	m0	$X + Y + Z$	M0
0 0 1	$\bar{X}\bar{Y}Z$	m1	$X + Y + \bar{Z}$	M1
0 1 0	$\bar{X}Y\bar{Z}$	m2	$X + \bar{Y} + Z$	M2
0 1 1	$\bar{X}YZ$	m3	$X + \bar{Y} + \bar{Z}$	M3
1 0 0	$X\bar{Y}\bar{Z}$	m4	$\bar{X} + Y + Z$	M4
1 0 1	$X\bar{Y}Z$	m5	$\bar{X} + Y + \bar{Z}$	M5
1 1 0	$XY\bar{Z}$	m6	$\bar{X} + \bar{Y} + Z$	M6
1 1 1	XYZ	m7	$\bar{X} + \bar{Y} + \bar{Z}$	M7

Example 1

- ▶ Formulate a logic function that fulfills the following truth table using
 - ▶ a) Minterms (SOP-form)
 - ▶ b) Maxterms (POS-form)

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

a) SOP-form

A	B	C	F	Minterm
0	0	0	0	
0	0	1	0	
0	1	0	1	$\bar{A}B\bar{C}$
0	1	1	0	
1	0	0	1	$A\bar{B}\bar{C}$
1	0	1	1	$A\bar{B}C$
1	1	0	0	
1	1	1	1	ABC

$$F = \bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C + ABC$$

b) POS-form

A	B	C	F	Maxterm
0	0	0	0	$A + B + C$
0	0	1	0	$A + B + \bar{C}$
0	1	0	1	
0	1	1	0	$A + \bar{B} + \bar{C}$
1	0	0	1	
1	0	1	1	
1	1	0	0	$\bar{A} + \bar{B} + C$
1	1	1	1	

$$F = (A + B + C)(A + B + \bar{C})(A + \bar{B} + \bar{C})(\bar{A} + \bar{B} + C)$$

Simplification of a logic function

- ▶ Logic functions presented in their normal forms do work, but they are often overtly complicated
- ▶ Usually it's possible to simplify the functions
- ▶ Minimization of a logic function is, in general, an NP-hard problem
 - ▶ Possible, but takes A LOT of time
- ▶ Minimization can still be done to some extent in reasonable time
- ▶ Tools that are used for this include:
 - ▶ Boolean algebra (simplification)
 - ▶ Karnaugh map ("K-map")
 - ▶ Certain computer software

Formulae of Boolean algebra

One-variable theorems:

$$X + 0 = X$$

$$X + 1 = 1$$

$$X + X = X$$

$$X + \bar{X} = 1$$

$$\overline{\bar{X}} = X$$

$$X \cdot 1 = X$$

$$X \cdot 0 = 0$$

$$X \cdot X = X$$

$$X \cdot \bar{X} = 0$$

Several-variable theorems:

$$X + Y = Y + X$$

$$X + (Y + Z) = (X + Y) + Z$$

$$X(Y + Z) = XY + XZ$$

$$XY = YX$$

$$X(YZ) = (XY)Z$$

$$X + YZ = (X + Y)(X + Z)$$

De Morgan's laws

$$\overline{X + Y} = \bar{X} \cdot \bar{Y}$$

$$\overline{X \cdot Y} = \bar{X} + \bar{Y}$$

Consensus theorem

- ▶ In addition to previously mentioned formulae, so called “consensus theorem” allows us to remove terms which are not needed:

$$AB + \bar{A}C + BC = AB + \bar{A}C$$


- ▶ Term BC is unnecessary. Why? Let's examine using set theory:

Consensus theorem

- ▶ In addition to previously mentioned formulae, so called “consensus theorem” allows us to remove terms which are not needed:

$$AB + \bar{A}C + BC = AB + \bar{A}C$$

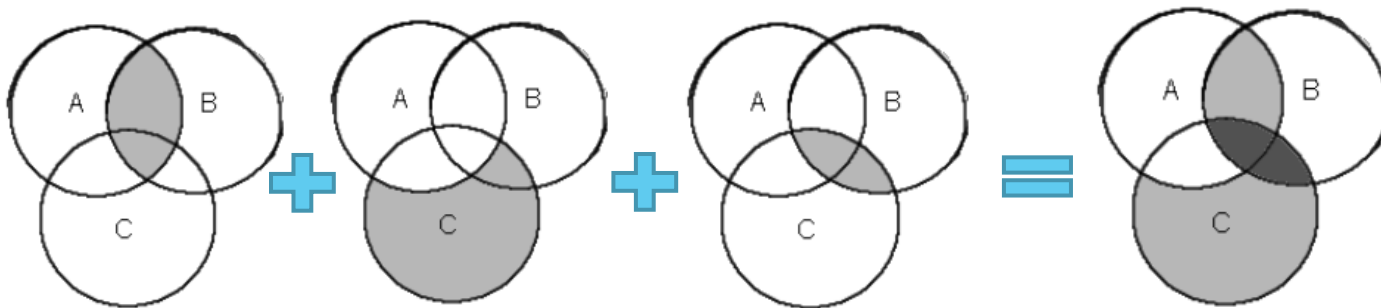- ▶ Term BC is unnecessary. Why? Let's examine using set theory:




Consensus theorem

- ▶ In addition to previously mentioned formulae, so called “consensus theorem” allows us to remove terms which are not needed:

$$AB + \bar{A}C + BC = AB + \bar{A}C$$

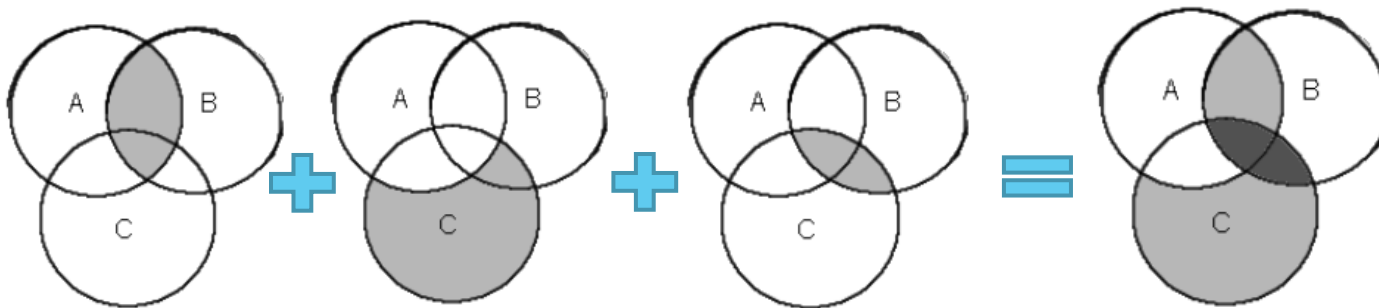- ▶ Term BC is unnecessary. Why? Let's examine using set theory:



- ▶ Area BC is colored twice; this means that it is already included in our chosen set. Therefore the term BC can left out.

Example 1 (continued)

- ▶ Simplify the logic functions of example 1 and present the circuit diagram in
 - ▶ a) SOP-form
 - b) POS-form.

Example 1 (continued)

- ▶ Simplify the logic functions of example 1 and present the circuit diagram in
 - ▶ a) SOP-form

$$***F = \bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C + ABC***$$

Example 1 (continued)

- ▶ Simplify the logic functions of example 1 and present the circuit diagram in

- ▶ a) SOP-form

$$\begin{aligned} F &= \bar{A}B\bar{C} + A\bar{B}\bar{C} + \textcolor{red}{A}\bar{B}C + ABC \quad \text{Duplication} \\ &= \bar{A}B\bar{C} + (A\bar{B}\bar{C} + \textcolor{red}{A}\bar{B}C) + (\textcolor{red}{A}\bar{B}C + ABC) \end{aligned}$$

Example 1 (continued)

- ▶ Simplify the logic functions of example 1 and present the circuit diagram in

- ▶ a) SOP-form

$$\begin{aligned} F &= \bar{A}B\bar{C} + A\bar{B}\bar{C} + \textcolor{red}{A\bar{B}C} + ABC && \text{Duplication} \\ &= \bar{A}B\bar{C} + (A\bar{B}\bar{C} + \textcolor{red}{A\bar{B}C}) + (\textcolor{red}{A\bar{B}C} + ABC) \\ &= \bar{A}B\bar{C} + A\bar{B}(\bar{C} + C) + AC(\bar{B} + B) \end{aligned}$$

Example 1 (continued)

- ▶ Simplify the logic functions of example 1 and present the circuit diagram in

- ▶ a) SOP-form


$$\begin{aligned} F &= \bar{A}B\bar{C} + A\bar{B}\bar{C} + \textcolor{red}{A}\bar{B}C + ABC && \text{Duplication} \\ &= \bar{A}B\bar{C} + (A\bar{B}\bar{C} + \textcolor{red}{A}\bar{B}C) + (\textcolor{red}{A}\bar{B}C + ABC) \\ &= \bar{A}B\bar{C} + A\bar{B}(\bar{C} + \textcolor{green}{C}) + AC(\bar{B} + \textcolor{green}{B}) && = 1 \\ &= \bar{A}B\bar{C} + A\bar{B} + AC \end{aligned}$$

Example 1 (continued)

- ▶ Simplify the logic functions of example 1 and present the circuit diagram in

- ▶ a) SOP-form
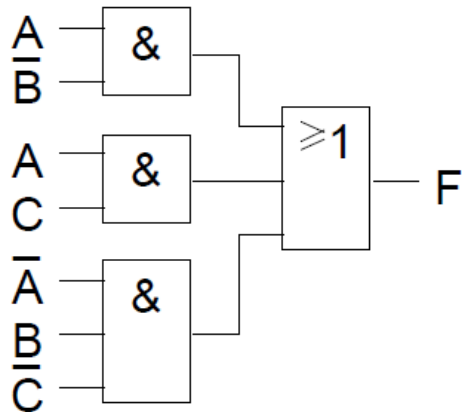
$$\begin{aligned} F &= \bar{A}B\bar{C} + A\bar{B}\bar{C} + \textcolor{red}{A}\bar{B}C + ABC && \text{Duplication} \\ &= \bar{A}B\bar{C} + (A\bar{B}\bar{C} + \textcolor{red}{A}\bar{B}C) + (\textcolor{red}{A}\bar{B}C + ABC) \\ &= \bar{A}B\bar{C} + A\bar{B}(\bar{C} + \textcolor{green}{C}) + AC(\bar{B} + \textcolor{green}{B}) && = 1 \\ &= \bar{A}B\bar{C} + A\bar{B} + AC \end{aligned}$$



Simplified circuit:
4 gates, 2+2+3+3
= 10 inputs

Example 1 (continued)

- ▶ Simplify the logic functions of example 1 and present the circuit diagram in
 - ▶ a) POS-form

Example 1 (continued)

- ▶ Simplify the logic functions of example 1 and present the circuit diagram in
 - ▶ a) POS-form

$$\mathbf{F = (A + B + C)(A + B + \overline{C})(A + \overline{B} + \overline{C})(\overline{A} + \overline{B} + C)}$$

Example 1 (continued)

- ▶ Simplify the logic functions of example 1 and present the circuit diagram in

- ▶ a) POS-form

Duplication

$$\begin{aligned} F &= (A + B + C)(A + B + \bar{C})(A + \bar{B} + \bar{C})(\bar{A} + \bar{B} + C) \\ &= (A + B + C)(A + B + \bar{C})(A + B + \bar{C})(A + \bar{B} + \bar{C})(\bar{A} + \bar{B} + C) \end{aligned}$$

Example 1 (continued)

- ▶ Simplify the logic functions of example 1 and present the circuit diagram in

- ▶ a) POS-form

Duplication

$$\begin{aligned} F &= (A + B + C)(A + B + \bar{C})(A + \bar{B} + \bar{C})(\bar{A} + \bar{B} + C) \\ &= \boxed{(A + B + C)(A + B + \bar{C})} \boxed{(A + B + \bar{C})(A + \bar{B} + \bar{C})} (\bar{A} + \bar{B} + C) \end{aligned}$$

Consensus theorem Consensus theorem

Example 1 (continued)

- ▶ Simplify the logic functions of example 1 and present the circuit diagram in

- ▶ a) POS-form

Duplication

$$\begin{aligned} F &= (A + B + C)(A + B + \bar{C})(A + \bar{B} + \bar{C})(\bar{A} + \bar{B} + C) \\ &= \boxed{(A + B + C)(A + B + \bar{C})} \boxed{(A + B + \bar{C})(A + \bar{B} + \bar{C})} (\bar{A} + \bar{B} + C) \\ &\quad \text{Consensus theorem} \qquad \text{Consensus theorem} \\ &= (A + B)(A + \bar{C})(\bar{A} + \bar{B} + C) \end{aligned}$$


Example 1 (continued)

- ▶ Simplify the logic functions of example 1 and present the circuit diagram in

- ▶ a) POS-form

Duplication
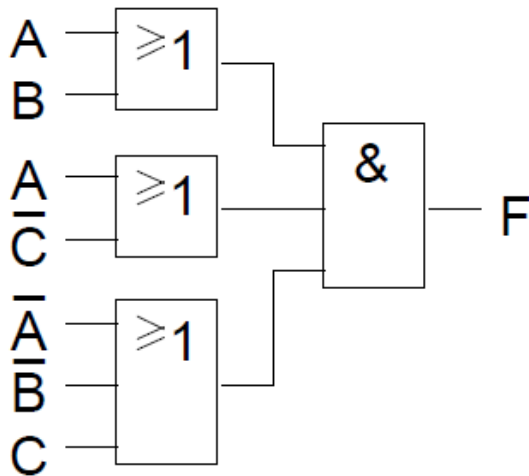
$$\begin{aligned} F &= (A + B + C)(A + B + \bar{C})(A + \bar{B} + \bar{C})(\bar{A} + \bar{B} + C) \\ &= \boxed{(A + B + C)(A + B + \bar{C})} \boxed{(A + B + \bar{C})(A + \bar{B} + \bar{C})} (\bar{A} + \bar{B} + C) \\ &\quad \text{Consensus theorem} \quad \text{Consensus theorem} \\ &= (A + B)(A + \bar{C})(\bar{A} + \bar{B} + C) \end{aligned}$$



Simplified circuit:
4 gates, 2+2+3+3
= 10 inputs

SOP or POS?

- ▶ Which normal form is easier, then?
- ▶ SOP is often considered “easier for brains”
 - ▶ No need to invert truth values
 - ▶ Easier to simplify (Boolean) algebraically
- ▶ The end result might be simpler in SOP- or POS-form
 - ▶ No way to tell unless you have a “trained eye”
- ▶ One heuristic approach:
 - ▶ In truth table, $F = 1$ for minterms and $F = 0$ for maxterms
 - ▶ If there are less minterms, SOP form gives a simpler starting point
 - ▶ If there are less maxterms, POS form gives a simpler starting point
 - ▶ ...but situation can change due to simplification!

Example 2

- ▶ Formulate a logic function that corresponds to the truth table on the right using both SOP and POS forms.
- ▶ Simplify your results.

A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

Example 2

- ▶ Formulate a logic function that corresponds to the truth table on the right using both SOP and POS forms.
- ▶ Simplify your results.



10 minterms, 6 maxterms. POS might be a smarter solution?

A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

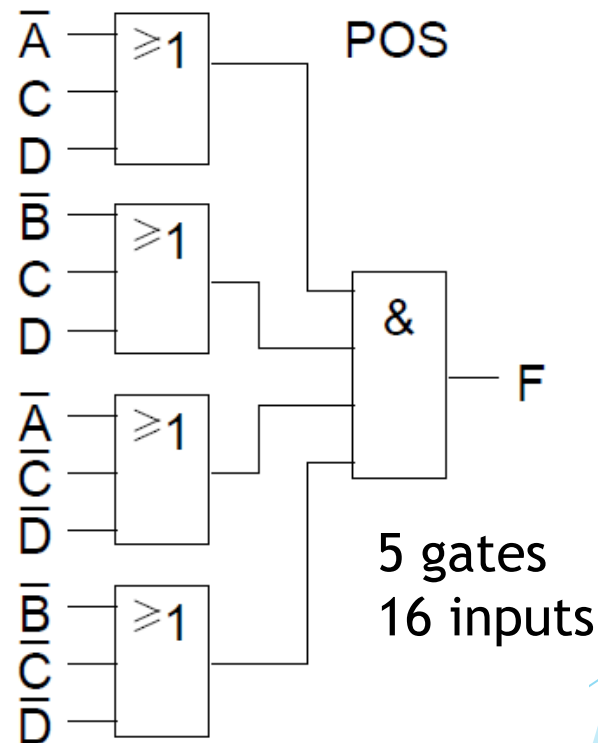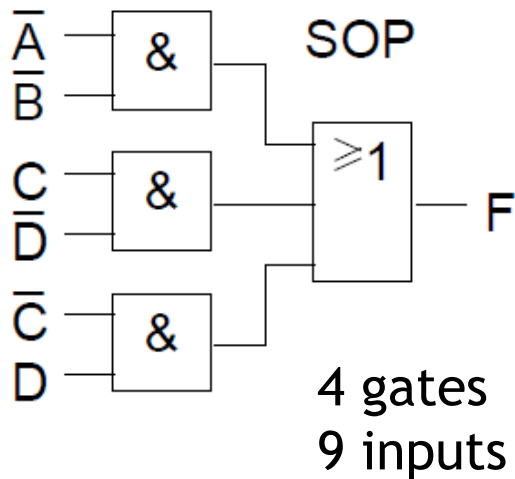Example 2

- ▶ When simplified, the situation is reversed:

$$F = \bar{A}\bar{B} + C\bar{D} + \bar{C}D \text{ (SOP)}$$



$$F = (\bar{A} + C + D)(\bar{B} + C + D)(\bar{A} + \bar{C} + \bar{D})(\bar{B} + \bar{C} + \bar{D}) \text{ (POS)}$$

Thank you!

